

國立高雄大學九十六學年度轉學招生考試試題

科目：工程數學
考試時間：90 分鐘

系所：電機工程學系
本科原始成績：100 分

是否使用計算機：是

1. (10%) Determine the equation is linear or nonlinear

(a) $\left(\frac{dy}{dx}\right)^2 + \sin x = 0$

(b) $(\sin x)\frac{d^2y}{dx^2} + (\cos x)\frac{dy}{dx} = e^x$

(c) $\frac{d^3y}{dx^3} + \sin y = 0$

(d) $(1-y)\frac{dy}{dx} + 2x = 0$

(e) $\frac{dy}{dx} = x^{1/2}y^{1/2}$

2. (10%) Solve $\frac{d^4y}{dx^4} + 4\frac{d^2y}{dx^2} + 4y = 0$

3. (10%) Solve the differential equation $\begin{cases} \frac{dx}{dt} = 3x - y \\ \frac{dy}{dt} = 2x \end{cases}$, given $x(0) = 3, y(0) = 4$

4. (10%) Solve $f(t) = te^t + \int_0^t \tau f(t-\tau) d\tau$ for $f(t)$

5. (10%) Solve $y'' + y = f(t)$, $y(0) = 0$, $y'(0) = 1$, where $f(t) = \begin{cases} 0, & 0 \leq t \leq 1 \\ 1, & 1 \leq t \leq 2 \\ 0, & t \geq 2 \end{cases}$

國立高雄大學九十六學年度轉學招生考試試題

科目：工程數學
考試時間：90 分鐘

系所：電機工程學系
本科原始成績：100 分

是否使用計算機：是

6. (10%) Find the solution of the following system
$$\begin{cases} w+2x-y+z=2 \\ -2w-3x-2y+2z=3 \\ 2w+6x+y-z=6 \end{cases}$$

7. (10%) λ_1, λ_2 and λ_3 are the eigenvalues of the matrix A

$$A = \begin{pmatrix} 3 & -3 & 2 \\ 1 & -1 & 2 \\ 1 & -3 & 4 \end{pmatrix}, \quad \lambda_1\lambda_2 + \lambda_2\lambda_3 + \lambda_3\lambda_1 = ?$$

8. (10%) For $A = \begin{pmatrix} 2 & 2 & 1 \\ 2 & 5 & 2 \\ 1 & 2 & 2 \end{pmatrix}$, Find a matrix P , such that $D = P^{-1}AP$ is diagonal.

9. (10%) $A = \begin{pmatrix} \cos \theta & -\sin \theta \\ \sin \theta & \cos \theta \end{pmatrix}$, compute A^{10}

10. (10%) Solve the initial-value problem, given $X' = \begin{pmatrix} 4 & -2 \\ 2 & -1 \end{pmatrix}X$, $X(0) = \begin{pmatrix} 7 \\ 5 \end{pmatrix}$

國立高雄大學九十六學年度轉學招生考試試題

科目：電路學
 考試時間：90 分鐘

系所：電機工程學系
 本科原始成績：100 分

是否使用計算機：是

1. (20%) Consider the circuit in Fig. P1.
 - (a) (15%) Write the mesh equations using the assigned currents.
 - (b) (5%) Find the mesh current I_1 .

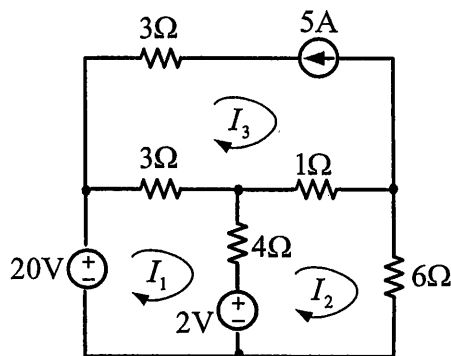


Fig. P1

2. (10%) Determine the Norton equivalent of the network in Fig. P2 at the terminals a-b.

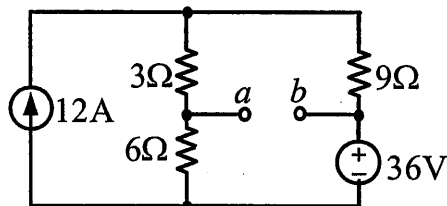


Fig. P2

3. (20%) Assume that the operational amplifier in Fig. P3 is ideal.
 - (a) (5%) Find v_A (the voltage at node A).
 - (b) (5%) Find the current supplied by the 9-V source.
 - (c) (5%) Find R_{in} (the input resistance seen by the 9-V source).
 - (d) (5%) Find the output voltage v_2 .

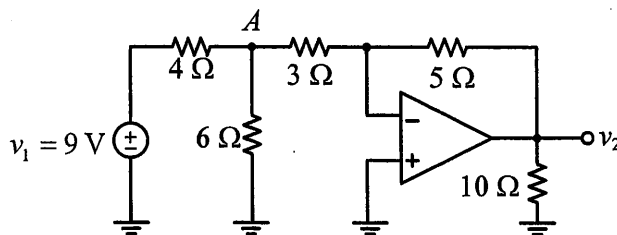


Fig. P3

國立高雄大學九十六學年度轉學招生考試試題

科目：電路學
 考試時間：90 分鐘

系所：電機工程學系
 本科原始成績：100 分

是否使用計算機：是

4. (10%) Consider the circuit in Fig. P4. The circuit is in steady state prior to time $t = 0$. The switch is opened at time $t = 0$. Obtain the capacitor voltage $v_C(t)$ for time $t > 0$.

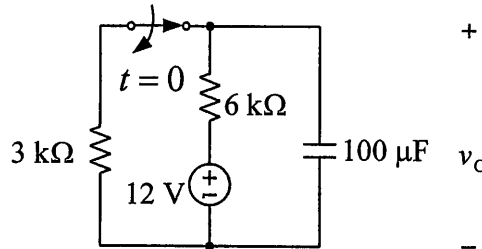


Fig. P4

5. (20%) Consider the two-port network in Fig. P5.
 (a) (10%) Find the z -parameters.
 (b) (10%) Find the y -parameters.

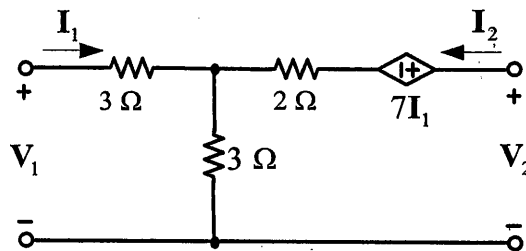


Fig. P5

6. (20%) The circuit shown in Fig. P6 consists of three loads in a series-parallel connection, with each of the loads defined as indicated.
 (a) (10%) Find the overall complex power of the circuit.
 (b) (5%) Find the overall power factor.
 (c) (5%) Find the phasor form of the source current I .

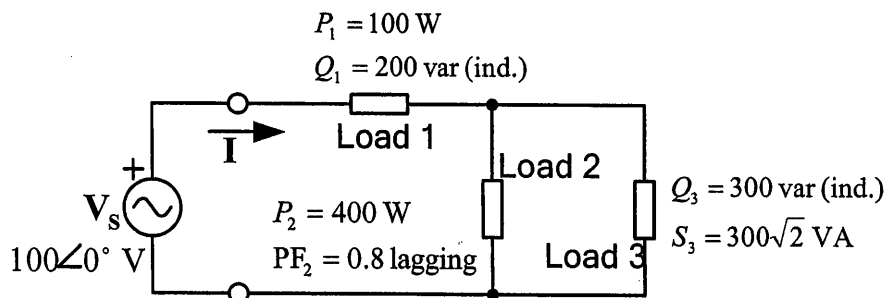


Fig. P6