

國立高雄大學九十八學年度轉學招生考試試題(轉3年級)

科目：工程數學
 考試時間：80分鐘

系所：電機工程學系
 本科原始成績：100分

是否使用計算機：是

- (1) Two vectors in a rectangular coordinate system are given by $A = 2a_x + 2a_y + 3a_z$ and $B = a_x + 2a_y + 2a_z$. Determine a vector $C = ma_x - 2a_y + na_z$, which is perpendicular to both A and B and has a length of 6 (10%)

- (2) Evaluate $\int_C x^2 y dx$, where the path of integration C is the quarter circle from (2,0) to (0,2) in Figure 1 (10%)

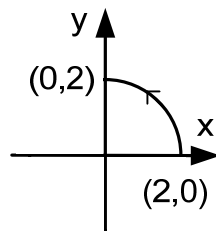


Figure 1

- (3) Find a,b,c and d so that the given function is analytic (10%)
 $f(z) = ax^2 + bxy - y^2 + i(-x^2 + cxy + dy^2)$

- (4) Find a linear mapping function $f(z)$ that maps from S onto S' (10%)
 S is a square with the vertices that are 0, 1, $1+i$ and i , from 1st to the 4th, respectively
 S' is a square with the vertices that are $-2+2i$, $-2-2i$, $2-2i$ and $2+2i$, from 1st to the 4th, respectively

- (5) Evaluate $\oint_C \frac{3z+2}{z^2+z} dz$ where C is the union of two closed curves in Figure 2 (10%)

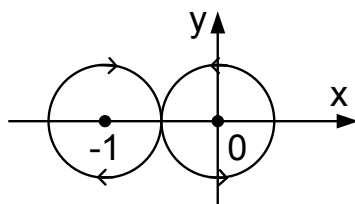


Figure 2

國立高雄大學九十八學年度轉學招生考試試題(轉3年級)

科目：工程數學
考試時間：80分鐘

系所：電機工程學系
本科原始成績：100分

是否使用計算機：是

(6) Find $y(x)$, given the initial value problem $y'' - 4y = 12x$, $y(0) = 4$, $y'(0) = 1$ (10%)

(7) Find $y(x)$, given the initial value problem $y'' + 2y' + 5y = \delta(t - 2\pi)$, $y'(0) = 0$, $y(0) = 0$ (10%)

(8) Solve $X' = \begin{pmatrix} 0 & 2 \\ -1 & 3 \end{pmatrix} X + \begin{pmatrix} 2t \\ 1 \end{pmatrix}$ (10%)

(9) Find the Fourier series of $f(x)$ (10%)

$$f(x) = \begin{cases} 0, & -2 < x < -1 \\ -1, & -1 \leq x < 0 \\ 1, & 0 \leq x < 1 \\ 0, & 1 \leq x < 2 \end{cases}$$

(10) If an 3×3 matrix product $AB=C$, where $A = \begin{bmatrix} 1 & 3 & 3 \\ 1 & 4 & 3 \\ 1 & 3 & 4 \end{bmatrix}$, $C = \begin{bmatrix} 1 & -1 & 1 \\ 2 & 1 & 0 \\ 0 & -1 & -2 \end{bmatrix}$, determine matrix B (10%)

國立高雄大學九十八學年度轉學招生考試試題(轉3年級)

科目：電路學
 考試時間：80 分鐘

系所：電機工程學系
 本科原始成績：100 分

是否使用計算機：是

1. (10%) Consider the two-terminal element with the v - i characteristic expressed by the function as

$$i(v) = 3v^2 + 2v + 1$$

where i is the current in ampere and v is the terminal voltage in volt.

- (a) (5%) Find the static resistance at $v = 2$ V.
 (b) (5%) Find the dynamic resistance at $v = 2$ V.

2. (15%) Consider the bridge network shown in Fig. P2.

- (a) (10%) Determine the equivalent resistance R_{ab} at terminals a - b .
 (b) (5%) Find i .

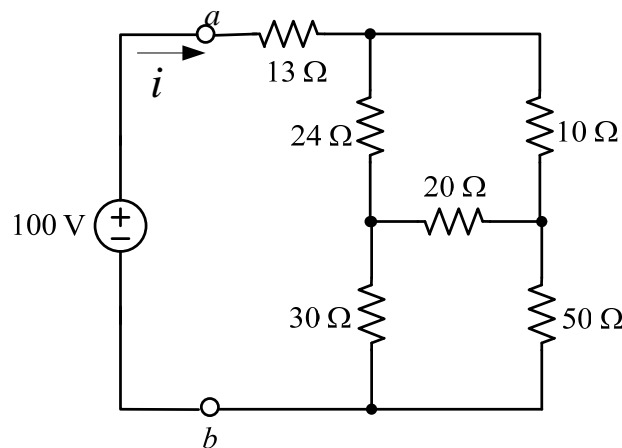


Fig. P2

3. (15%) Consider the circuit shown in Fig. P3.

- (a) (9%) Write a set of node-voltage equations.
 (b) (6%) Determine the node voltages v_1 , v_2 , and v_3 .

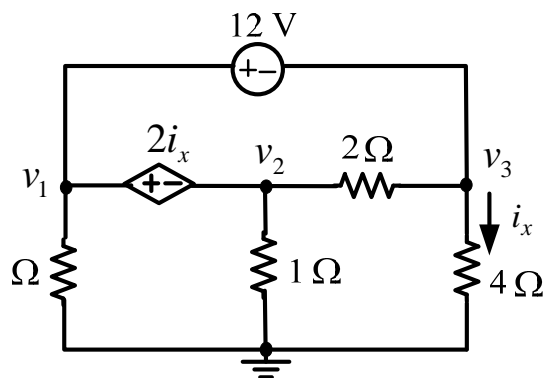


Fig. P3

國立高雄大學九十八學年度轉學招生考試試題(轉3年級)

科目：電路學
 考試時間：80分鐘

系所：電機工程學系
 本科原始成績：100分

是否使用計算機：是

4. (15%) Sketch the straight-line approximation of the Bode plot for the following transfer function.

$$H(s) = \frac{10^{10} s}{(s + 10^3)(s + 10^5)}$$

5. (15%) Consider the parallel RLC circuit in Fig. P5. Assume that $v(0) = 5\text{ V}$, $i(0) = 0\text{ A}$, $L = 1\text{ H}$, $C = 10\text{ mF}$, and $R = 5\text{ }\Omega$. Find $v(t)$ for $t \geq 0$.

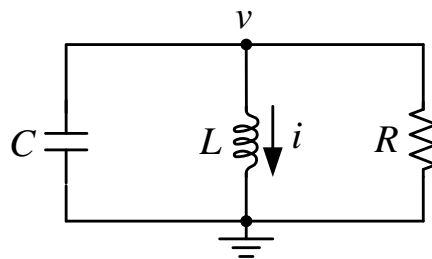


Fig. P5

6. (15%) Use *source transformation* to find the current I_o in Fig. P6.

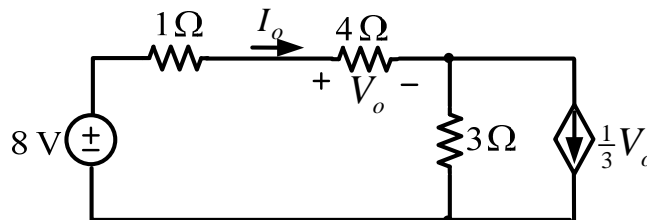


Fig. P6

7. (15%) The constants R and L of a coil can be obtained by connecting the coil in series with a known resistance and measuring the coil voltage V_x , the resistor voltage V_1 , and the total voltage V_T (Fig. P7). The frequency must also be known, but the phase angles of the voltages are not known. Given that $\omega = 100\text{ rad/s}$, $V_1 = 10\text{ V}$, $V_x = 20\sqrt{5}\text{ V}$, and $V_T = 50\text{ V}$, find R and L .

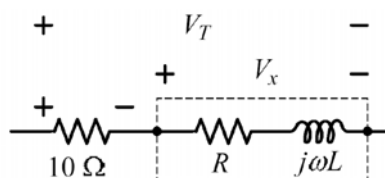


Fig. P7